

T_{eaching} L_{ondon} C_{omputing}

Programming for GCSE

Topic 9.2: Circuits for Adding



COMPUTING AT SCHOOL
EDUCATE · ENGAGE · ENCOURAGE



SUPPORTED BY
MAYOR OF LONDON



Aims

- Show how computers are built from logic gates
- Circuit for Adding
 - ... two inputs
 - ... three inputs – one column
 - ... many columns

Key Idea:

- Represent numbers as binary digits
 - Digits as logic levels
-

HALF ADDER

Half Adder

- Simplest circuit for binary addition
 - input: two bits A and B
 - output: sum S and carry C
- Sums \rightarrow ? \rightarrow circuit



$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 0 \text{ carry } 1$$

Example:



Half Adder – Truth Table

- Binary addition – truth table
 - input: two bits A and B
 - output: sum S and carry C

A	B	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Quiz: Determine the formula for S and C

Half Adder – Formula

- Simplest circuit for binary addition
 - input: two bits A and B
 - output: sum S and carry C

A	B	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S = \overline{A}.B + A.\overline{B}$$


$$C = A.B$$

Quiz: draw the circuit

Half Adder – Circuit

- Simplest circuit for binary addition
 - input: two bits A and B
 - output: sum S and carry C

A	B	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0


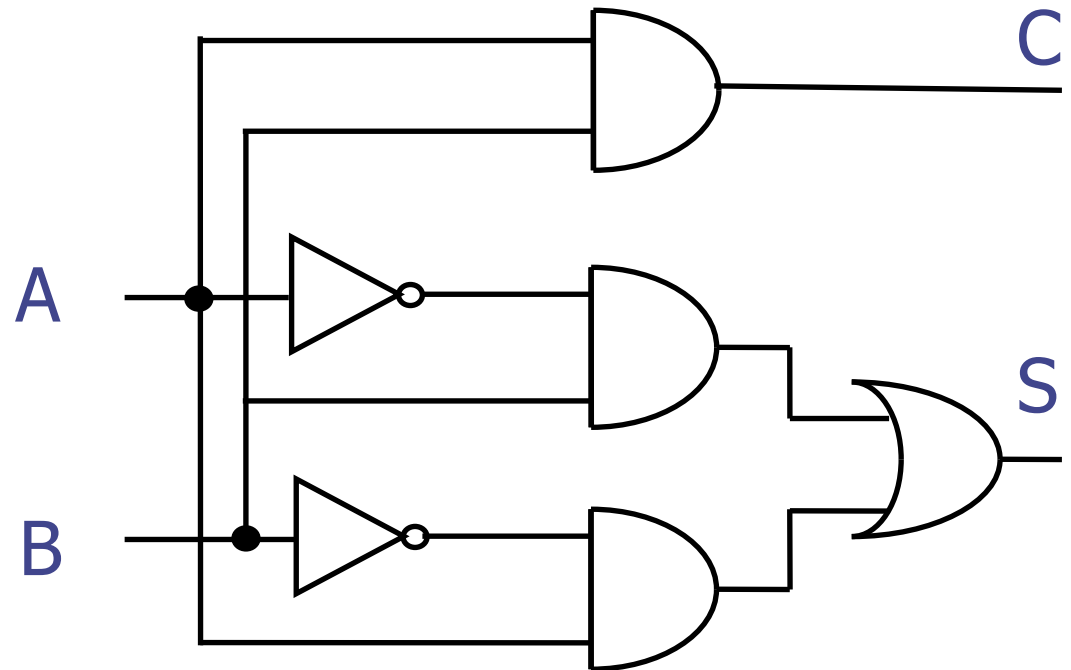


FULL ADDER

One Columns of a Binary Addition

Full Adder – One Column

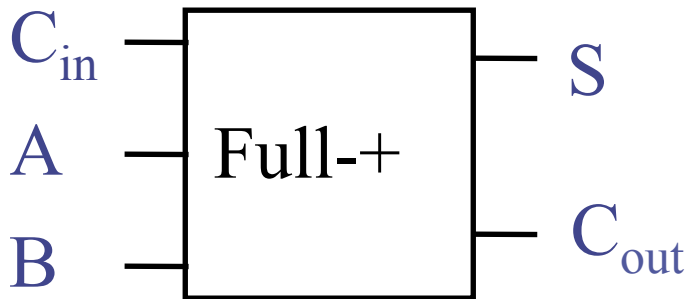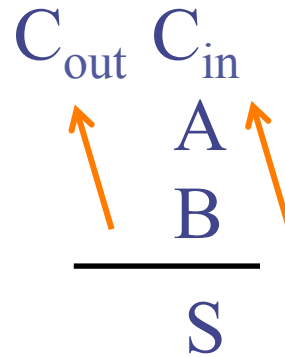
- Each digit (column) of binary add has 3 inputs
 - A, B and carry C_{in}



A	B	C_{in}	C_{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


Full-Adder from 2 Half Adders

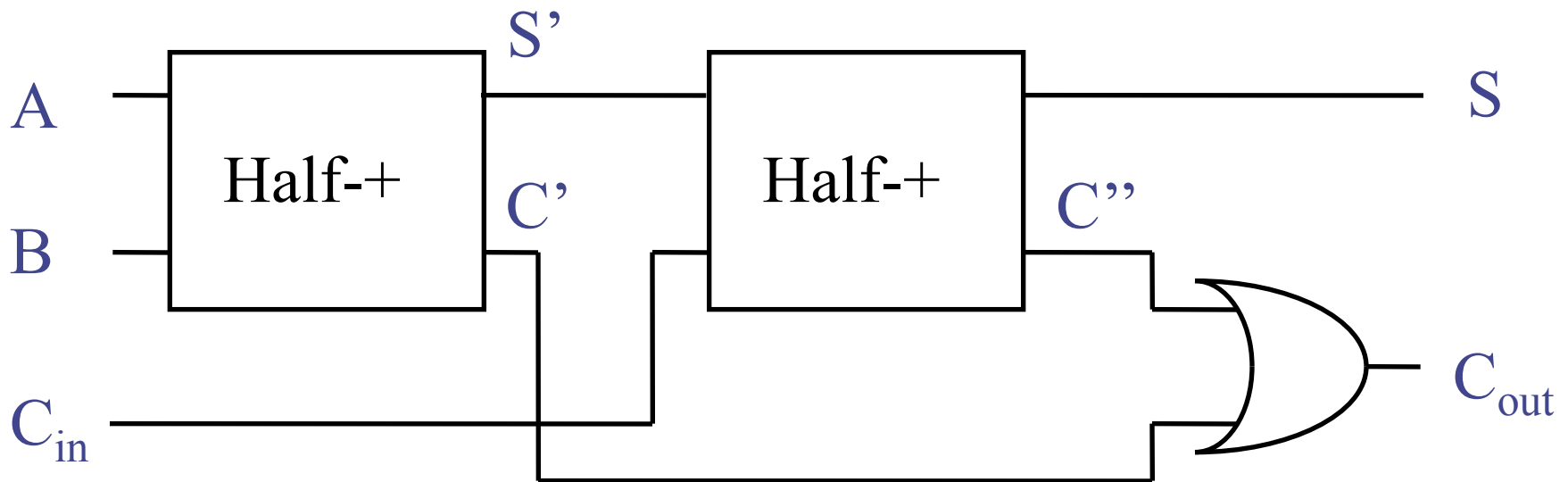- Step 1: add $A + B$
- Step 2: add carry to result
- Step 3: carry




Ripple Adder

- Add each bit, carry from previous bit

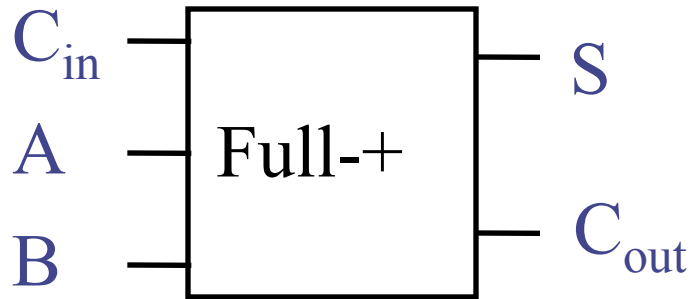

Ripple Adder

- Add each bit, carry from previous bit

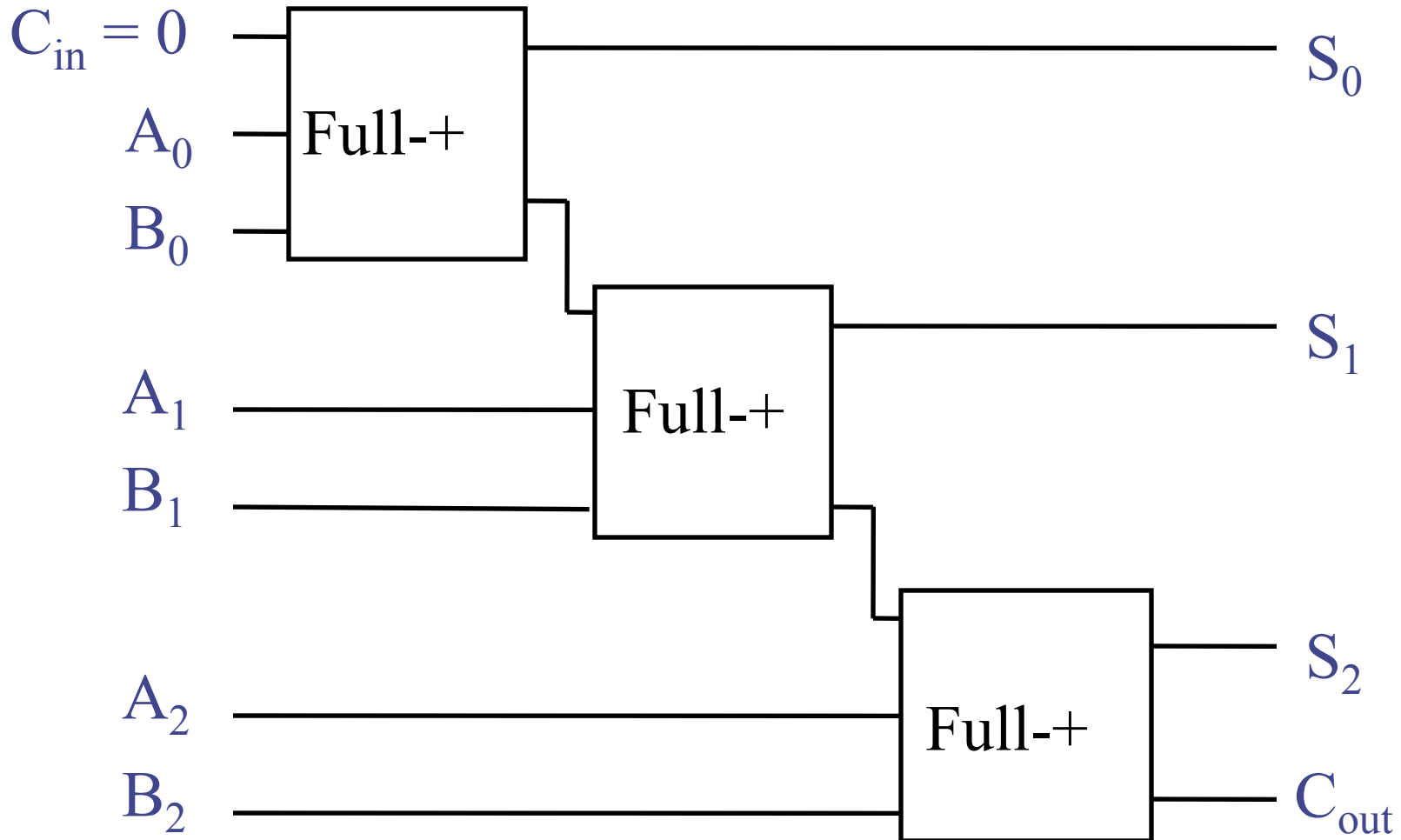



SYLLABUS

Syllabus – Binary

- GCSE (OCR)
 - Logic circuits: and, or , not
 - Truth tables
 - Writing boolean expressions
- AS/A2 (AQA)
 - (AS) More boolean algebra
 - (AS) More gates

Joined up view?

How to make sense of logic unless used e.g. adder circuit.

binary → truth table
→ circuit

Summary

- Show how logic circuits build a computer
 - Binary digits become logic inputs
 - Circuits operate on numbers
 - Adder stages
 - One column, no carry
 - One column, with carry
 - Many columns
-